

Automatic Street Light Control System

① LDR [Light dependent Resistor]

↳ A passive sensor whose resistance changes with light intensity.

Working Principal:

Light photons $\rightarrow$ $\uparrow$ charge carriers $\rightarrow$ $\downarrow$ resistance

(Bright light $\rightarrow$ low R)
(Darkness $\rightarrow$ High R)

~~② Voltage Divider~~

LDR is used in voltage divider

$$V_{out} = V_{cc} \cdot \frac{R}{R + LDR}$$

Converts lights $\rightarrow$ analog voltage

② ADC0804 [Analog to digital converter]

8bit ADC

analog voltage (0-5V) to digital (0-255)

why needed? [microprocessor only works on digital data]

V_{int}/V_{in} - Input

DO-D7 - output data

WR - start conversion

RD - read data

INTR - conversion complete

CLK IN - clock in

Working steps:

WR = LOW (start conversion)

ADC process light

INTR = LOW → done

RD = LOW → data available on D0-D7

(3) 8085 Microprocessor

8 bit data bus

16 bit address bus → 64KB

Operates on +5V

ALE → separates address / data

IO/M → memory or I/O

RD / WR → Control signals

INTR → interrupt from ADC

- Reads ADC value

- Compares with the threshold

- Controls street light

(4) Latches

→ ADD - AD7 multiplexed

→ use Latch to store address

ALE = high [Latch stores address]

ALE = low [output remains fixed]

(5) Memory [EPROM + RAM]

→ Permanent memory

→ Stores program

→ temporary memory
→ stores temporary data

(6.) ULN2003 (Driver IC)
 → Darlington transistor array [7 channels]

Purpose: Amplifies current

Why Needed:

8085 Output → Very low current
 Relay needs higher current to ON

Working:

Input high → output sinks current → relay ON.

(7.) Relay
 → Electrically operated Switch

Working:

coil Energized → contacts switch

(8.) 8255 PPI
 → Acts as bridge between 8085 and External world.

Handles:

- Input from ADC0804
- Output to ULN2003

Port A (PA0 - PA7) reads 8-bit data.

Port B (PB0 - PB7) connected to ULN.

Mode-0 (simple I/O mode)

Step-by-step working of project

Step-1 Initialization
8085 sends Control word → Configures 8255

Step-2 Read Light Data
Light photons → Bright / Dark → LR / HR

Data transfer to 8085
8255 reads data from port A
8085 triggers read
INTR LOW
ADC converts

Step-3 Decision-making

if value < threshold → Dark
Else Light

Step-4 Output Control
8085 writes to PORT B of 8255
Eg PBO = 1 → Relay ON → Light ON
PBO = 0 → Relay off → Light OFF

Signal flow
ADC → Port A (8255) → 8085 → Port B (8255) → U/LN
Light ← Relay

Assumption:
8255 mapped as I/O Ports
Port A → 00H
Port B → 01H
Port C → 02H
Control signal → 03H
Control word = 82H

8085 Program:
Initialize 8255: MVI A, 82H
OUT 03H (Control word)
START: IN 00H (read ADT)
CPI 80H (compare)
JC DARK
MVI A, 00H (PBO = 0, Light off)
OUT 01H
JMP START
DARK: MVI A, 01H
OUT 01H
JMP START (PBO = 1, Light = on)